

FIT1047 - Week 3

Central Processing Units, Part 2



FIT1047

Monash University

Recap

In the previous lecture we saw

- Basic CPU architecture
- MARIE assembly code
- Combinational circuits (in particular: adders)

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder


FIT1047


Monash University

Overview

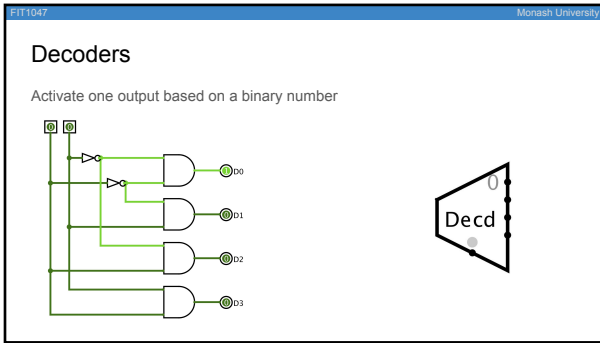- Arithmetic / Logic Units (ALUs)
- Sequential circuits
 - Flip flops, registers, counters
 - memory
- Control
 - Executing a program



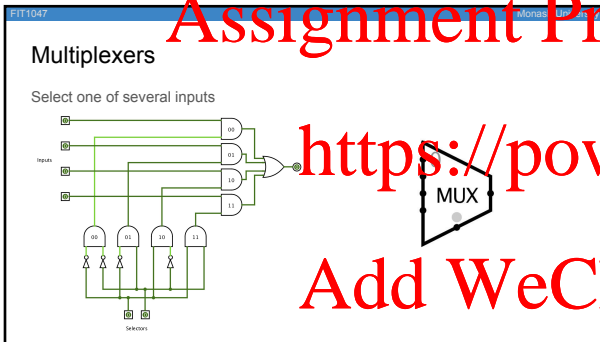

 

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

FIT1047
Monash University

ALU

Implements basic computations:

- Integer addition, subtraction (in more complex CPUs: multiplication)
- Comparisons
- Bitwise Boolean operations (AND, OR, NOT)
- Shifting

Inputs:

- Two n -bit **operands**
- Op-code (determines the operation to perform)

Output:

- n -bit result and status flags (overflow? error?)

FIT1047
Monash University

ALU

How does the circuit decide which operation to perform?


- Simply do all in parallel
- Then choose the result prescribed by the op-code

Sounds like a job for a MUX!

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

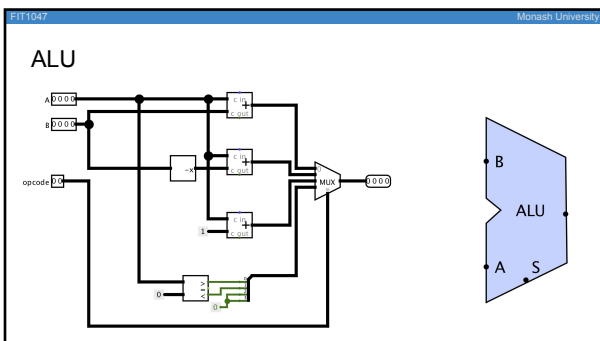

Sequential Circuits


(output depends on *sequence* of inputs)

FT11047 Monash University

Sequences

How can a circuit "remember" the past?

Feed the output back into the input!



Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

FT11047 Monash University

Sequences

Toggle using another input

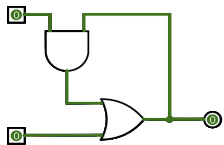

FIT1047
Monash University

Set/reset latch

But digital circuits use a single bit for data!

FIT1047
Monash University

D flip-flop

- Two inputs:
 - The bit to be stored
 - A signal: read or write mode
- One output:
 - The bit currently stored

FIT1047
Monash University

Registers

- Very fast memory inside the CPU
- Some special purpose registers
 - PC, IR, MBR, MAR (for MARIE)
- Some general purpose registers
 - AC (MARIE), AH/AL, BH/BL, CH/CL, DH/DL (x86)
- Fixed bit width
 - E.g. 16 bit in MARIE
 - 16/32 or 64 bits in modern processors

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

FIT1047
Monash University
Register file

- Collection of registers
- Each implemented using n flip-flops (for n bits)
- n inputs and outputs
- Additional input: which register to write to
- Additional input: which register to read from

FIT1047
Monash University
Register file

FIT1047
Monash University
MARIE architecture

FT11047Monash University

Control Unit

- Controls fetch-decode-execute cycle
- Switches *control signals* on and off:
 - Each signal is a "wire" inside the CPU
 - Which register to read/write
 - Which memory address to read/write
 - Which operation to perform in the ALU
- Needs to "know" which signals to switch on/off for each instruction

Let's specify, for each instruction, what to do!

FT11047Monash University

Register Transfer Language (RTL)

- Break down instructions into small steps
- CPU performs one step per *clock cycle*
- Each step transfers data between registers and/or memory.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

FT11047Monash University

RTL: fetch

1. $MAR \leftarrow PC$	<i>load PC into memory address register</i>
2. $MBR \leftarrow M[MAR]$	<i>load value from memory (M) into memory buffer</i>
3. $IR \leftarrow MBR$	<i>load value from MBR into instruction register</i>
4. $PC \leftarrow PC+1$	<i>increment PC to point at next instruction</i>

FIT1047
Monash University

RTL: decode

5. $MAR \leftarrow X$

load address X from IR into MAR

6. $MBR \leftarrow M[MAR]$

load value from memory into MBR

Some instructions need both of these steps, some just step 5, some instructions need neither 5 nor 6.

FIT1047
Monash University

RTL: execute

Depends on the concrete instruction (of course).

Example: Add X

7. $AC \leftarrow AC + MBR$

(place result of addition in AC)

Example: Jump X

6. $PC \leftarrow MAR$

(load X, stored in MAR, into PC)

FIT1047
Monash University

RTL: Full Add X instruction

- $MAR \leftarrow PC$
- $MBR \leftarrow M[MAR]$
- $IR \leftarrow MBR$
- $PC \leftarrow PC + 1$
- $MAR \leftarrow X$
- $MBR \leftarrow M[MAR]$
- $AC \leftarrow AC + MBR$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

FIT1047
Monash University

Control Signals

Each RTL step tells us which control signals to switch on and off.

Example: $MBR \leftarrow M[MAR]$
(load memory value from address stored in MAR into MBR)

- Switch register file to write into MBR
- Switch memory into read mode

FIT1047
Monash University

Control Signals

Each RTL step tells us which control signals to switch on and off.

Example: $AC \leftarrow AC + MBR$
(add value in MBR to value stored in AC, store result in AC)

- Switch register file to read from AC
- Switch register file to write into AC
- Switch ALU into "Add" mode (ALU always reads one operand from MBR)

FIT1047
Monash University

Outlook

Tutorials this week:

- MARIE programming
- Circuits for adding and subtracting

Next lecture:

- More MARIE instructions
- Memory
- Input/Output and Interrupts

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder